

Quiz #5: Ohm's Law

Name: _____

For the circuit shown, you know that:

$$R_1 = 400 \, \Omega$$

$$R_2 = 300 \, \Omega$$

$$R_3 = 1200 \, \Omega$$


Also, you know that the current through resistor 2 is:

$$I_2 = 10.0 \, \text{mA}$$

Note carefully which side is the “long” side for the **power supply!**

Determine the five quantities that are listed in the box.

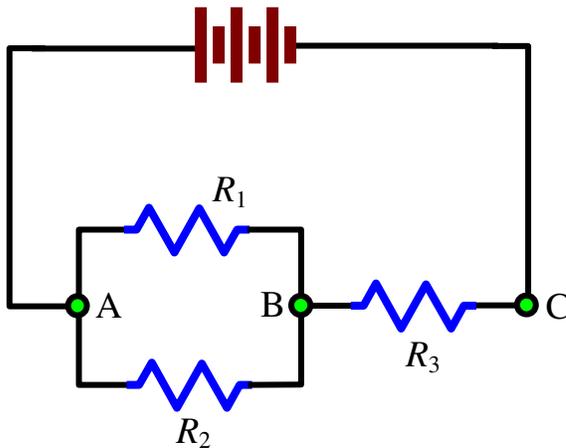Each of the 5 questions is a one step problem, but you'll usually use a prior answer to get the next one! Some questions require Ohm's Law, and some require Kirchhoff's Node Law.



$$V_A - V_B =$$

$$I \text{ through } R_1 =$$

$$I \text{ through } R_3 =$$

$$V_B - V_C =$$

$$V_A - V_C =$$