


Analytical Physics Lab, Worksheet #4: DC Circuits & Kirchhoff's Laws

Name: _____


Date of Lab: _____

Partner: _____


II. Voltage Measurements		I. Current Measurements	
$V_A - V_G$	V	I_{CD}	mA
$V_A - V_B$	V	I_{EF}	mA
$V_B - V_C$	V	I_{GH}	mA
$V_C - V_D$	V	I_{AB}	mA
$V_D - V_E$	V		
$V_E - V_F$	V	R_1	Ω
$V_F - V_G$	V	R_2	Ω
$V_G - V_A$	V		
$V_B - V_E$	V		

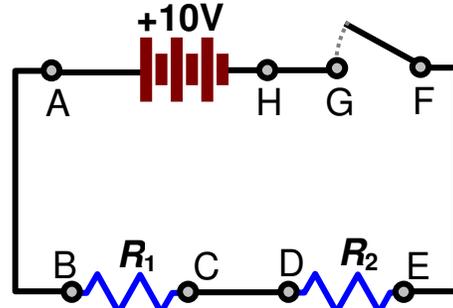

IV. Voltage Measurements		III. Current Measurements	
$V_A - V_J$	V	I_{GH}	mA
$V_C - V_E$	V	I_{EG}	mA
$V_D - V_F$	V	I_{FG}	mA
$V_A - V_B$	V	I_{AB}	mA
$V_E - V_J$	V		
$V_J - V_A$	V	R_1	Ω
		R_2	Ω

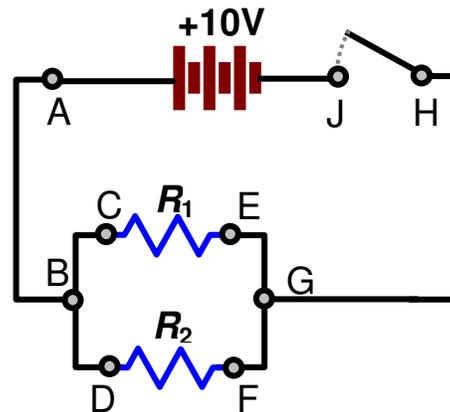

V. Voltage Measurements		V. Current Measurements	
$V_A - V_K$	V	I_{HJ}	mA
$V_C - V_E$	V	I_{EG}	mA
$V_D - V_F$	V	I_{FG}	mA
$V_G - V_H$	V	I_{AB}	mA
$V_B - V_H$	V		
$V_K - V_A$	V	R_1	Ω
		R_2	Ω
		R_3	Ω

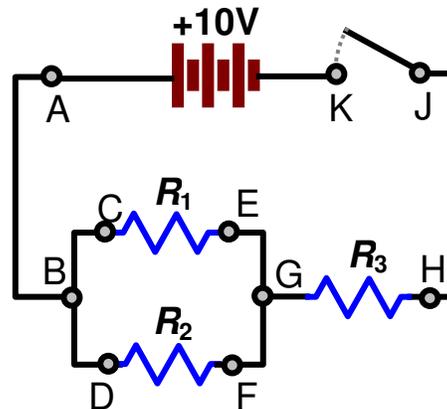

Consider a node having two connections, like node H in the last circuit.

What is the relationship between currents I_{GH} and I_{HJ} ?

Use a formula, and check your signs.

Rewrite your previous answer in terms of I_{GH} and I_{HJ} instead of I_{GH} and I_{JH} .

Similarly, consider a node having three (or more) connections, like node G in the last circuit. What is the relationship between currents I_{EG} , I_{FG} , and I_{HG} ?